



School of Electrical and Computer Engineering
University of Newcastle, Australia

ELEC3251

Assignment 2

**Analysis of Switching Harmonics,
Grid Connected Inverters and
Space Vector Control System Design**

Liam Patey-Dennis
c3349900

1 PV Voltage and Switching Harmonics

1.1 Method

To determine the correct switching output, a test was performed at the H-bridge output to confirm that both switching strategies can be achieved. This test involved setting a constant sinusoid input at the H-bridge controller.

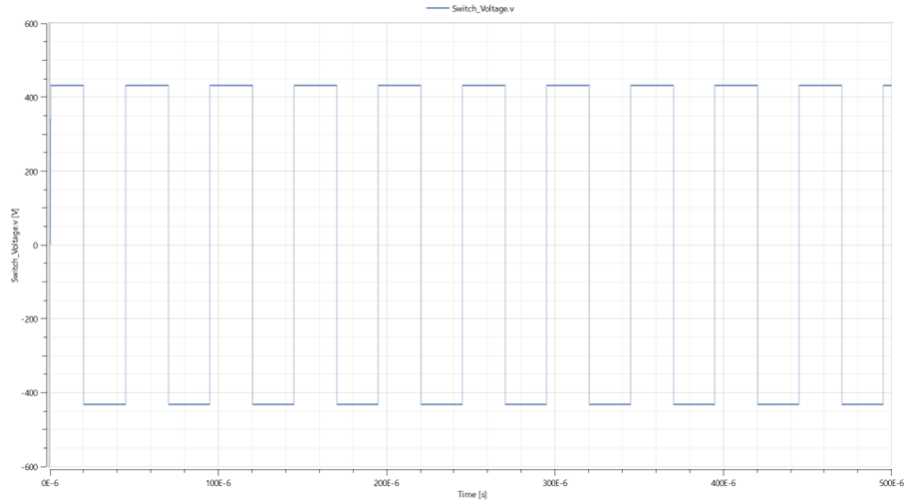


Figure 1: Bipolar Switching Test

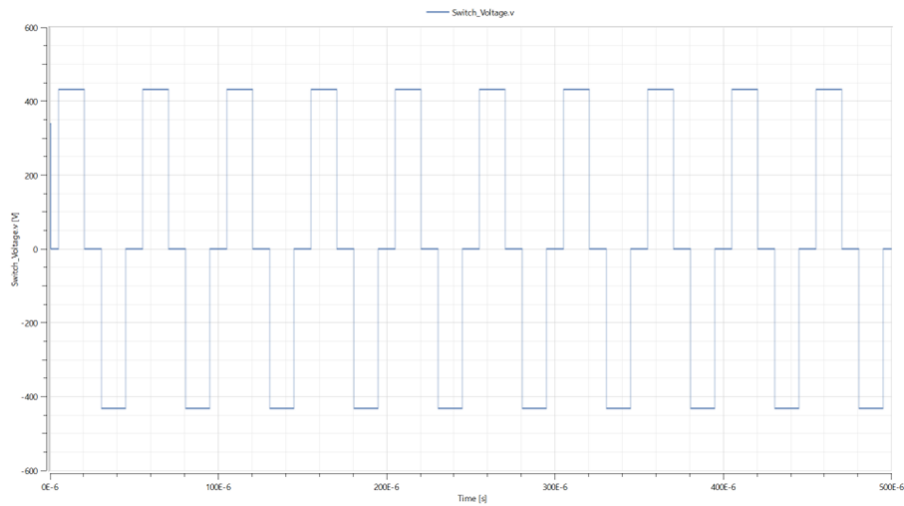


Figure 2: Unipolar Switching Test

The switching frequency was set to 20 kHz . The current sensor, Ic was added to measure

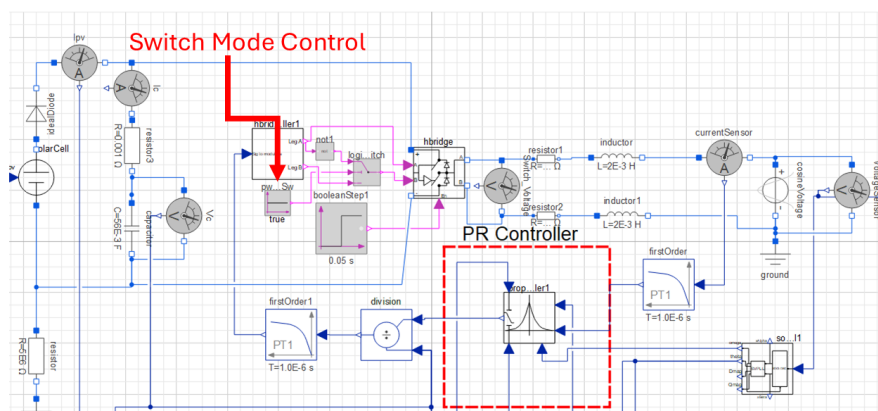


Figure 3: How to set bipolar and unipolar switching

current through the capacitor. The voltage sensor for the capacitor was named Vc. The simulation was run twice, at 0.2 s and at 10 s. This allows the viewing of different frequency components. The numbers of cells in series for the solar cell was 850. The capacitance was set to 56 mF. The some experimentation, it was found that the input supply was 5kW.

1.2 Results

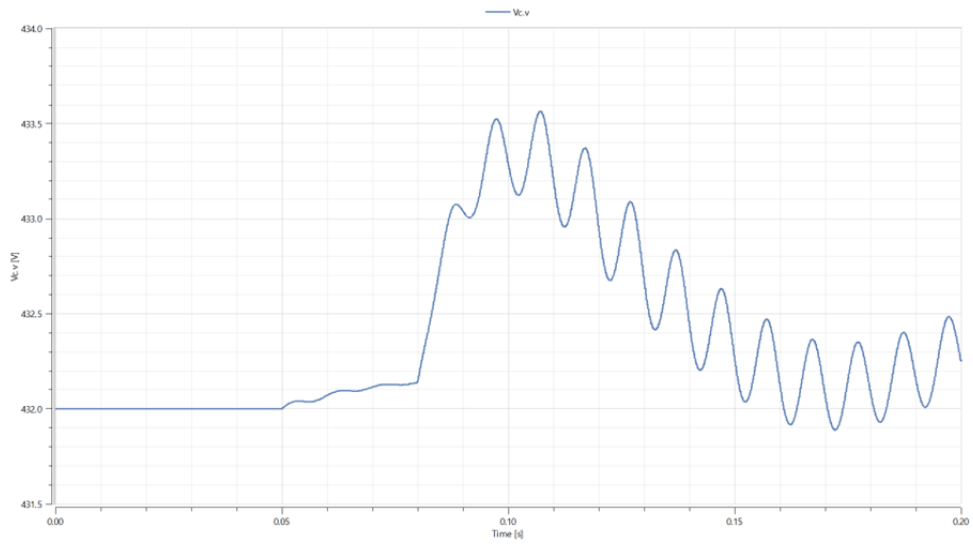


Figure 4: Bipolar V_c , capacitor voltage (PV to GND), Sim Time = 0.2 s

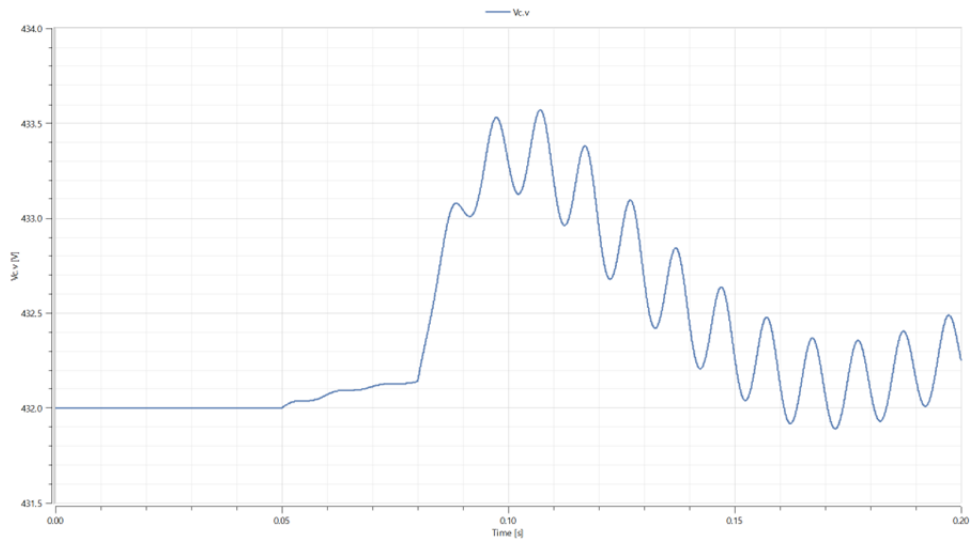


Figure 5: Unipolar V_c , capacitor voltage (PV to GND), Sim Time = 0.2 s

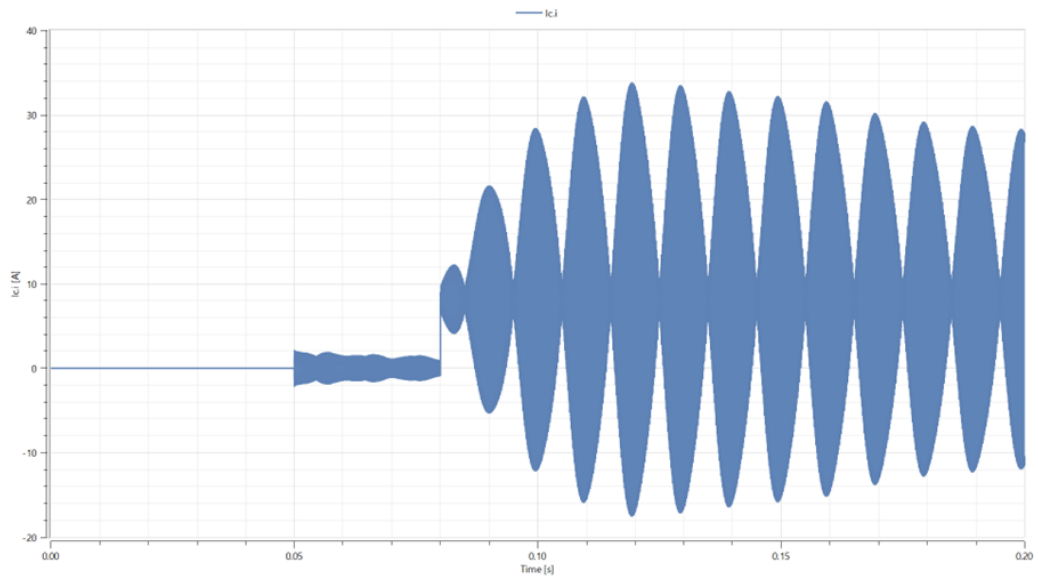


Figure 6: Bipolar I_c , current through capacitor, Sim Time = 0.2 s

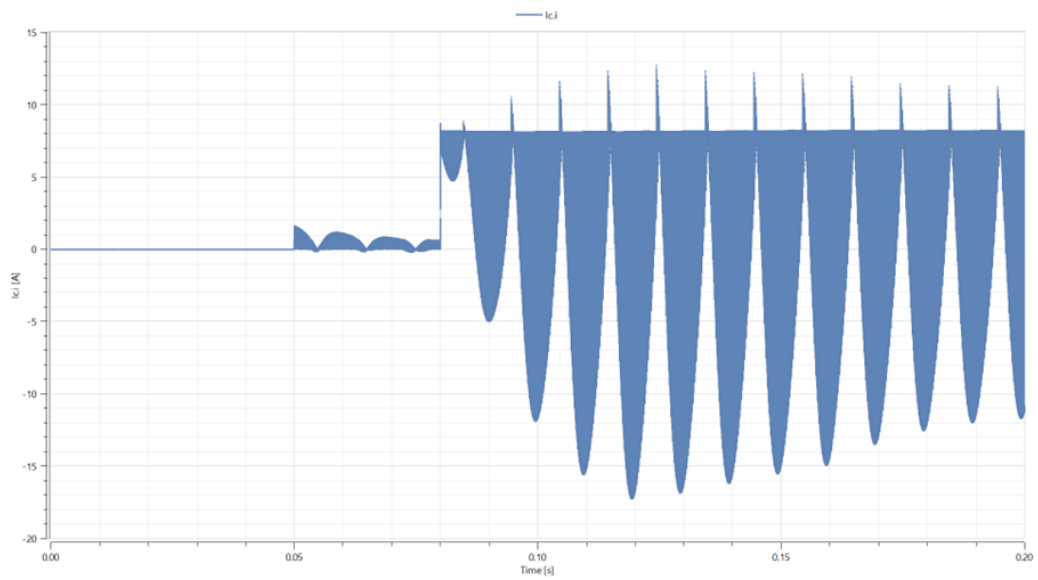


Figure 7: Unipolar I_c , current through capacitor, Sim Time = 0.2 s

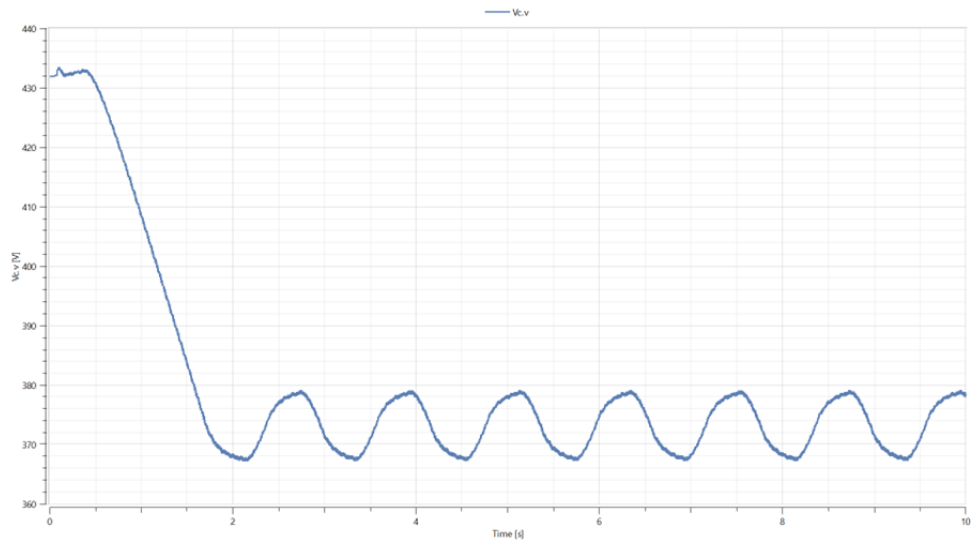


Figure 8: Bipolar V_c , capacitor voltage (PV to GND), Sim Time = 10 s

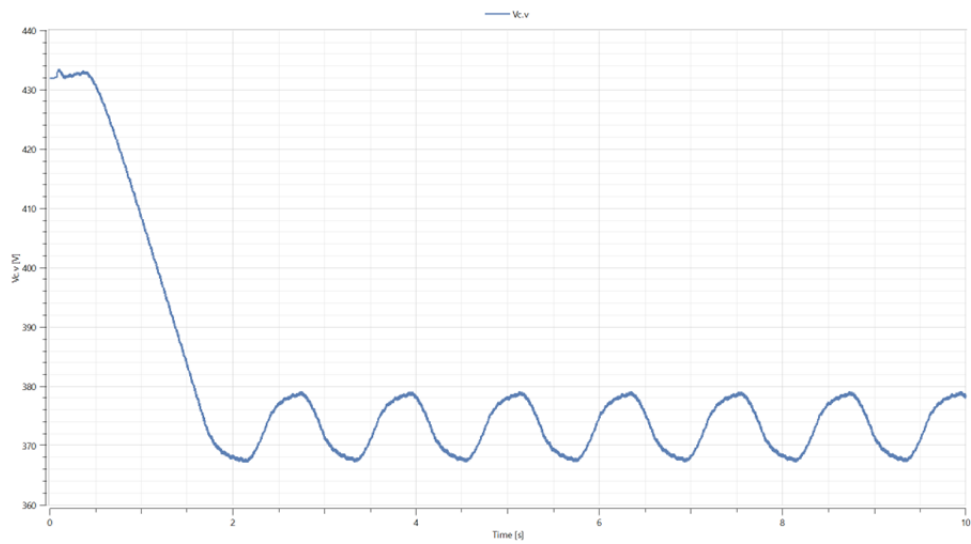


Figure 9: Unipolar V_c , capacitor voltage (PV to GND), Sim Time = 10 s

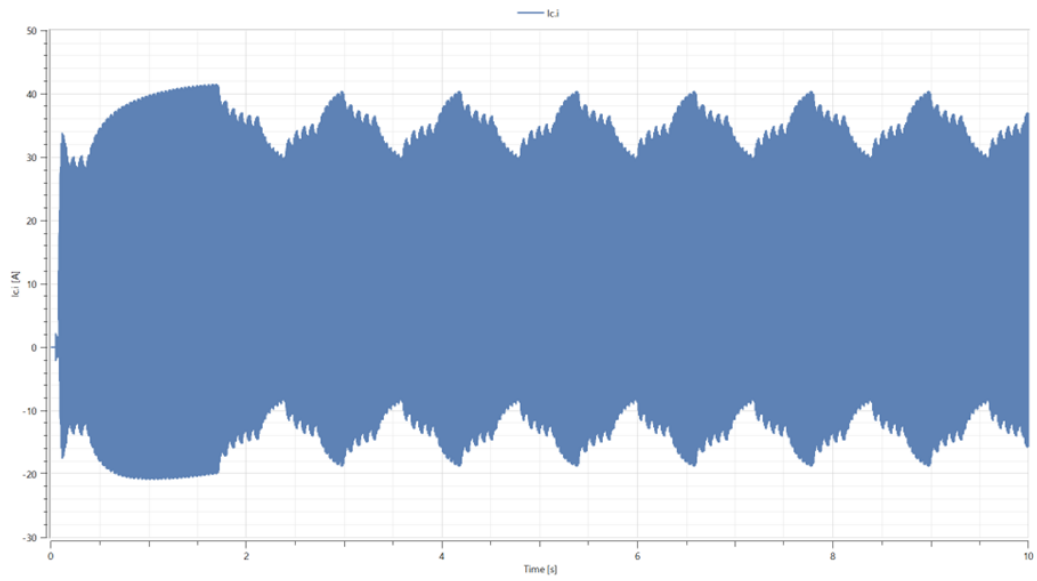


Figure 10: Bipolar I_c , current through capacitor, Sim Time = 10 s

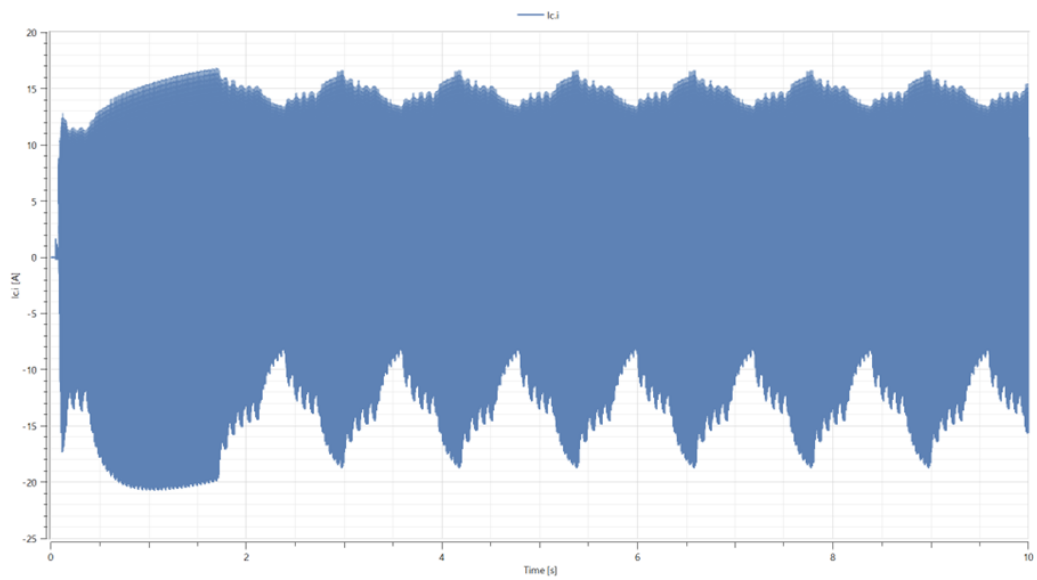


Figure 11: Unipolar I_c , current through capacitor, Sim Time = 10 s

1.3 Discussion

Comparing both switching methods, the capacitor voltage (PV) was basically equal, see Figure 4. At time 0.05 s the H-bridge starts switching to produce a current. In the 10s simulation, 8, a steady state of

This frequency component can be calculated by measuring its period, which is inferred from Figure 4 is about 0.01 s. For wave relationship,

$$f = \frac{1}{T} \quad (1)$$

Therefore the frequency, f , is 100 Hz . This comes from the grid connected voltage. This is 50 Hz , that makes this signal, the second harmonic. The same frequency can be seen from the current plots, Figure 6. There is a distinct difference between the plots, due to the different switching modes, see Figure 7. This is expected, as harmonic disturbance should be less under unipolar switching. The greatest piece of evidence, can be inferred from the magnitudes of the current plots. As the magnitude of the harmonics is from 40 to -20 for bipolar and from 15 to -20 for unipolar.

2 Grid Connected Inverters

References